

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 199235

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. II) THEORY EXAMINATION 2013-14

ELECTRICAL ENGINEERING

Time : 3 Hours

Total Marks : 100

Note :- Attempt all Sections. Assume missing data if any.

SECTION-A

1. Answer all parts of this Section : (2×10=20)

- (a) State the Superposition and Norton's theorem _____.
- (b) A sinusoidal current having rms value of _____ is to another sinusoidal current of rms value of _____. The rms value of resultant current is _____.
- (c) Which of the following condition is common to both series and parallel resonance ?
 - (i) Current is maximum
 - (ii) Power is low
 - (iii) Impedance is minimum
 - (iv) P.F. is unity
- (d) Enlist the type of moving iron instrument.
- (e) Which of the following formula is used to express active power in balanced 3- ϕ circuit :
 - (i) $V_L I_L \cos \phi$


- (ii) $\sqrt{3} V_L I_L \cos \phi$
 (iii) $V_{ph} I_{ph} \cos \phi$
 (iv) $\sqrt{3} V_{ph} I_{ph} \cos \phi$
- (f) If the frequency of the excitation mmf is 'f'. The hysteresis loss and eddy current loss is proportional to _____ respectively.
- (g) Draw and explain hysteresis loop.
- (h) A 3- ϕ induction motor has 4-pole runs at 4% slip and full load. If speed of the motor is 720 rpm, the supply frequency is _____.
- (i) In armature winding of a 4-pole, lap wound DC machine having 760 active conductors and running at 1200 rpm with 20 mwb flux per pole, the induced voltage will be _____.

(j) Match the following :


Type of motor	Application
DC series motor	Centrifugal pumps
Synchronous motor	Cranes
3- ϕ Squirrel cage IM	Hair dryer
1-f Shaded pole motor	Condense

SECTION-B

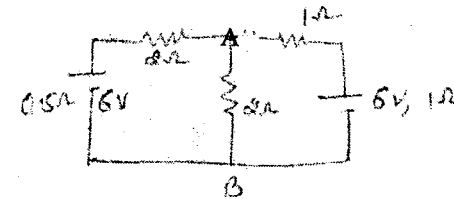2. Answer any **four** parts of this Section : (10×4=40)
- (a) Using superposition theorem, calculate the current in the AB branch in the circuit shown in below figure :



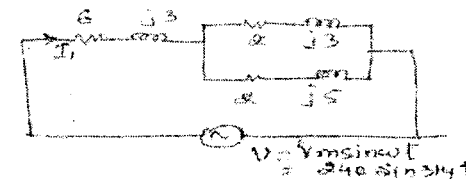- (b) 1. An alternating voltage is $V = 100 \sin 100 t$; find :
- Amplitude
 - Time period and frequency
 - Angular velocity
 - Form factor
 - Crest factor.
2. Refer to the circuit shown in the following figure find :
- rms line current
 - power dissipated
 - power factor.



- (c) Explain two wattmeter method of determine power in 3- ϕ system. Discuss the variation in readings for different power factor of load from unit to zero.

- (d) Explain construction and working principle of the following:
- I- ϕ induction type energy meter
 - PMMC type measuring instrument.
- (e) 1. Draw single line diagram of a power system generating station and user. Mention the different voltage levels.
2. Describe the analogies that can be made between electric and magnetic circuit.
- (f) The ohmic values of the circuit parameters of a transformer having a turn ratio of 5, are $R_1 = 0.5 \text{ ohm}$, $R_2 = 0.021 \text{ ohm}$, $X_1 = 3.2 \text{ ohm}$, $X_2 = 0.12 \text{ ohm}$, $R_0 = 350 \text{ ohm}$, referred to the primary and $X_m = 98 \text{ ohm}$ referred to the primary. Draw the approximate equivalent circuits of the transformer referred to secondary. Show the numerical values of the circuit parameters.

SECTION-C

3. Answer any **four** parts of this Section : (10×4=40)
- (a) Determine the current I_x and I_y in the following network. State theorem used.
- (b) 1. A balance delta-connected load of impedance $16 + j 12 / \text{phase}$ is connected to a 3- ϕ 400 V supply. Find the phase current, line current, power factor, power, reactive VA, total VA.
2. A moving coil milli-ammeter having a resistance of 8 ohm gives full scale deflection when a current of 5 mA is passed through it, explain how this instrument can be used for measurement of
- Current upto 2A
 - Voltage upto 8V.

- (c) A DC shunt generator delivers 50 kW at 250 V when running at 500 rpm. The armature and field resistance are 0.05 ohm and 125 ohm respectively. Calculate the speed of the same machine and developed torque when running as a shunt motor and taking 50 kW at 250 V. Allow 1 volt per bursh for contact drop.
- (d) Explain the various methods of starting of a 1- ϕ induction motor.
- (e) Explain the following characteristics of a DC shunt motors :
- Speed – armature current
 - Torque – armature current
 - Speed – torque.
- (f) Define slip in 3- ϕ induction motor. What is its value at starting and at the synchronous speed ? Draw torque-slip characteristics of 3- ϕ induction motor.