

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 199211

Roll No.

--	--	--	--	--	--	--	--	--	--

**B.Tech.****(SEM. II) THEORY EXAMINATION 2013-14****ELECTRONICS ENGG.****Time : 3 Hours****Total Marks : 100****Note :- Attempt all Sections.****SECTION-A**

1. All parts are compulsory. Write short answers by giving proper reasons. : (2×10=20)
  - (a) Calculate the dynamic forward and reverse resistance of a PN junction diode when the applied voltage is 0.25 V at  $T = 300^\circ \text{K}$  given  $I_0 = 2 \mu\text{A}$ .
  - (b) Distinguish between avalanche and zener mechanisms.
  - (c) Draw the block diagram of unregulated Power Supply.
  - (d) Establish the relationship between  $I_{\text{CBO}}$  and  $I_{\text{CEO}}$ .
  - (e) Draw the transfer and output characteristic of Tunnel Diode.
  - (f) Enlist the difference between JFET and MOSFET.
  - (g) An operational Amplifier has a differential gain of 103 and a CMRR of 100, input voltages are 120  $\mu\text{V}$  and 80  $\mu\text{V}$ . Determine the output voltage.
  - (h) The BJT circuit has  $I_c = 10 \text{ mA}$  and  $\alpha = 0.98$ . Determine the value of  $I_E$ .
  - (i) In JFET  $I_{\text{DSS}} = 8\text{mA}$ ,  $V_p = -4\text{V}$  biased at  $V_{\text{GS}} = -1.8\text{V}$ . Determine the value  $g_m$ .
  - (j) What are Lissajous figure ?

## SECTION-B

2. Attempt any three parts of the following : (10×3=30)

- (a) (i) Draw and explain the working of Bridge rectifier with input and output waveforms. Calculate efficiency and ripple factor for the same.
- (ii) For the network shown in Fig. 1, determine the output voltage.

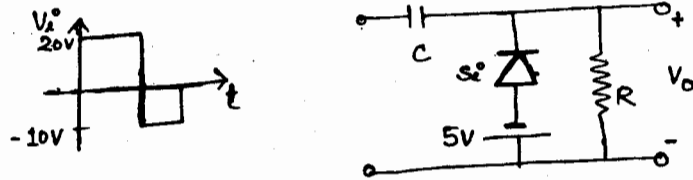


Figure 1

- (b) (i) With proper circuit diagram, draw the Base curve and collector curves of n-p-n transistor in C-E configuration.
- (ii) Determine  $I_{CQ}$  and  $V_{CEQ}$  for the network shown in Fig. 2.

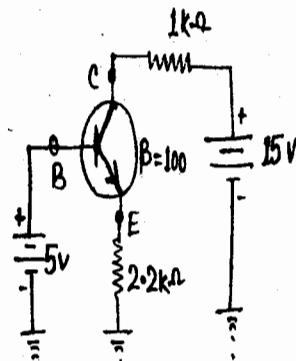


Figure 2

- (c) (i) With suitable ckt. diagram describe the working of n-channel JFET with drain and transfer curves.
- (ii) Draw the dc load line and determine  $V_G$ ,  $I_{DQ}$ ,  $V_{GSQ}$  for the network shown in Fig. 3.

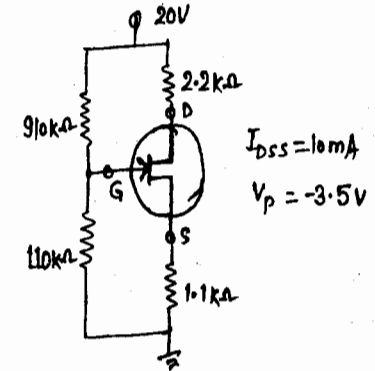


Figure 3

- (d) (i) How OP-Amp acts as a differentiator ? Derive its output voltage expression.
- (ii) Determine the output voltage for the network shown in Fig. 4.

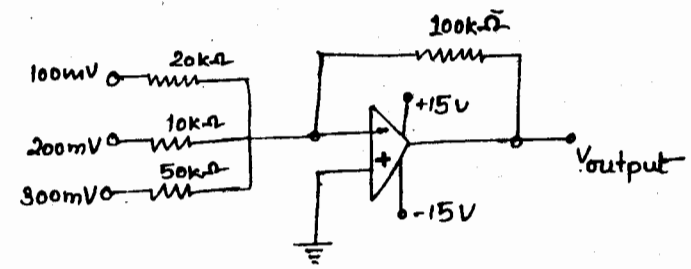


Figure 4

- (e) (i) Write short note on digital multimeter with proper block diagram.
- (ii) For the given zener diode network shown in Fig. 5 determine  $V_L$ ,  $V_R$ ,  $I_Z$  and  $I_R$ .

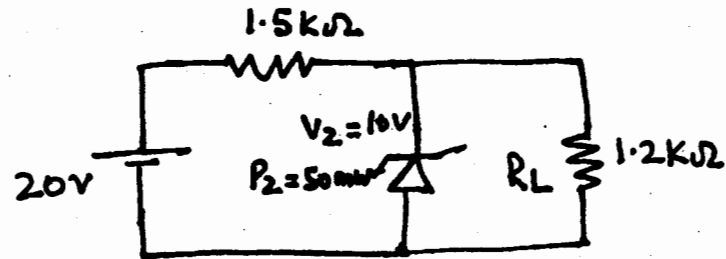


Figure 5

### SECTION-C

Note : Attempt all questions of this section. (10×5=50)

3. Attempt any two parts of the following :
- (a) Determine the output voltage for given network in Fig. 6.

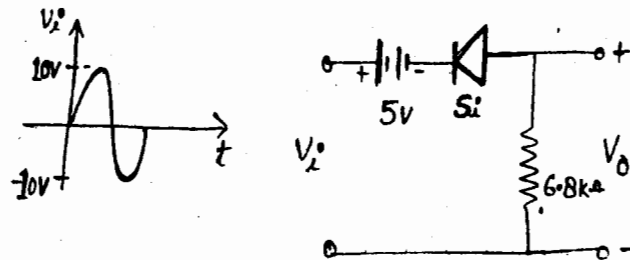


Figure 6

- (b) Design a clamper to perform the function indicated in following Fig. 7.

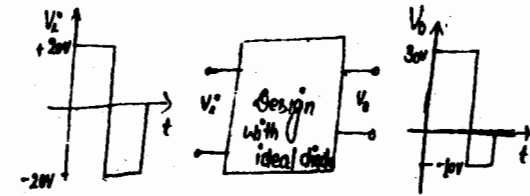


Figure 7

- (c) Explain Schottky diode and varicap with their applications.
4. Attempt any two parts of the following :
- (a) Draw and explain the a.c. equivalent circuit of voltage divider Bias amplifier using re model.
- (b) Determine the voltage Gain of emitter follower in Fig. 8.
- If  $\beta = 150$ , what is a.c. input voltage ?

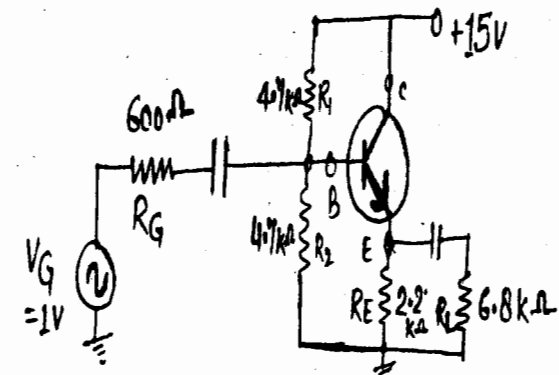


Figure 8

- (c) Calculate the voltage Gain of VDB amplifier shown in Fig. 9.

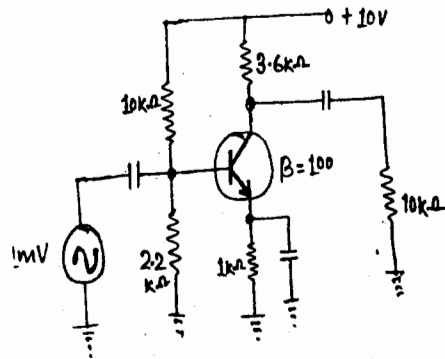


Figure 9

5. Attempt any two parts of the following :

- (a) With proper circuit diagram draw and explain the drain and transfer characteristic curve for N-Channel JFET.

Show that  $\epsilon_m = \frac{-2}{V_p} \sqrt{I_{DSS} I_{DS}}$

- (b) For the network shown in Fig.10, calculate  $V_G$ ,  $V_{GS}$ ,  $I_D$ ,  $V_{DS}$  and  $V_s$ .

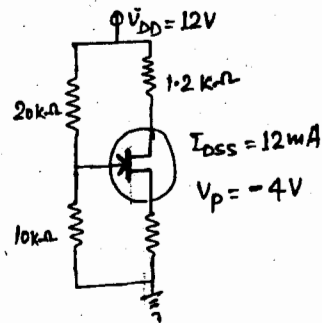


Figure 10

- (c) Determine the output voltage of following network shown in Fig. 11. having  $V_{GS(off)} = -2V$ ,  $I_{DSS} = 4mA$  and  $g_{mo} = 3000 \mu S$

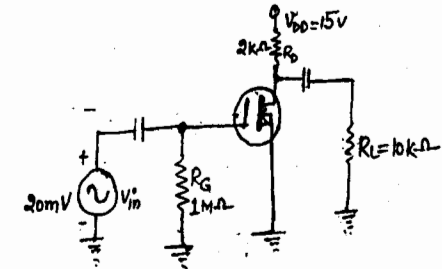


Figure 11

6. Attempt any two parts of the following :

- (a) Define CMRR, Slew Rate and concept of virtual ground in Op-AMP.

- (b) For the network shown in Fig. 12., determine the output voltage.

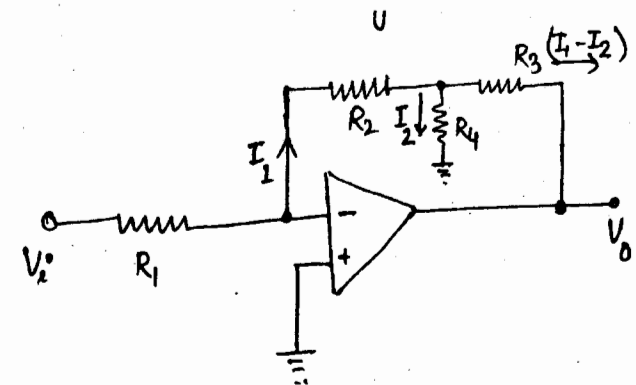


Figure 12

(c) Determine output voltage for network in Fig. 13.

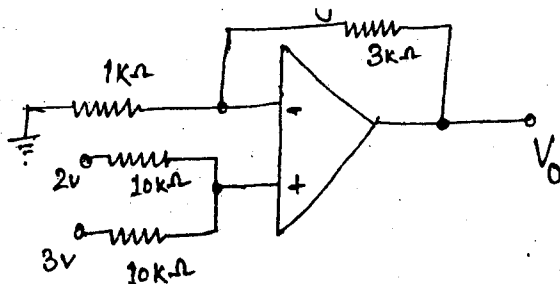


Figure 13

7. Attempt any **two** parts of the following :

- Draw the block diagram of function generator and explain its working.
- Draw the block diagram of CRO and explain the function of each block.
- How phase and frequency of an input signal is measured using CRO ?