

Printed Pages : 7



EE-301

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 121301**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B. Tech.**

(SEM. III) (ODD SEM.) THEORY  
EXAMINATION, 2014-15

**NETWORK ANALYSIS AND SYNTHESIS**

Time : 3 Hours]

[Total Marks : 100

Note : Attempt ALL questions.

1 Attempt any four parts : 5×4=20

(a) For a incidence matrix A given below, draw the oriented graph :

$$A = \begin{bmatrix} 0 & 0 & 1 & 1 & 1 & 1 & 0 & 1 & 0 & 0 \\ 0 & -1 & -1 & 0 & 0 & 0 & -1 & 0 & 0 & -1 \\ -1 & 1 & 0 & 0 & 0 & 0 & 0 & -1 & -1 & 1 \\ 1 & 0 & 0 & 0 & -1 & -1 & 1 & 0 & 0 & 0 \end{bmatrix}$$

(b) Explain following terms with reference to network topology :

- (i) Tree
- (ii) Co-tree
- (iii) Incidence matrix
- (iv) Oriented graph
- (v) Twig and link.

(c) For the network shown in Fig. 1 shown below draw the directed graph. And also find number possible tree.

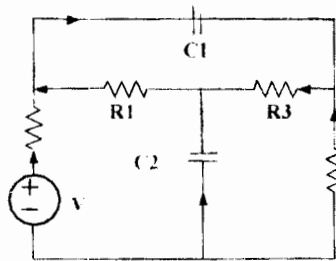


Fig.1

(d) For the network shown in Fig. 2 shown below :

- (i) Draw the directed graph
- (ii) F-cutset matrix.

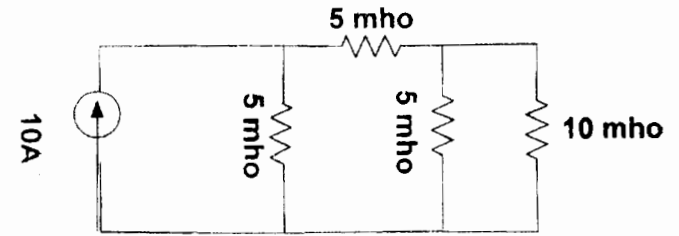


Fig. 2

- (e) State the principle of duality. Explain the graphical method to draw dual network.
- (f) The fundamental cutset matrix is given as :

				<i>Twig</i>	<i>Link</i>					
				1	2	3	4	5	6	7
$Q =$	1	0	0	0	-1	0	0	0	0	0
	0	1	0	0	1	0	1	1	1	1
	0	0	1	0	0	1	1	1	1	0
	0	0	0	1	0	1	1	0	0	0

Draw the oriented graph.

2 Attempt Any Three Questions :

$$6 \frac{2}{3} \times 3 = 20$$

- (a) State and prove Millman's theorem for the n voltage sources connected in parallel.

- (b) State and explain compensation theorem with suitable example.
- (c) Determine the current in capacitor C, by the principle of superposition of the network shown below in Fig.3

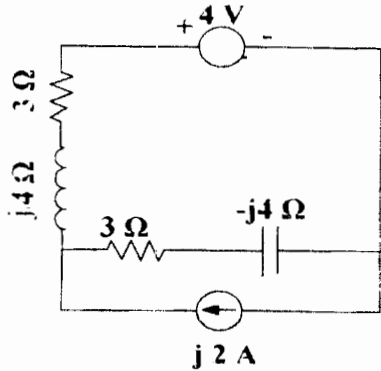


Fig.3.

- (d) Determine the maximum power which can be absorbed by a pure resistive load when placed across the output terminal a, b of the network shown below in Fig. 4.

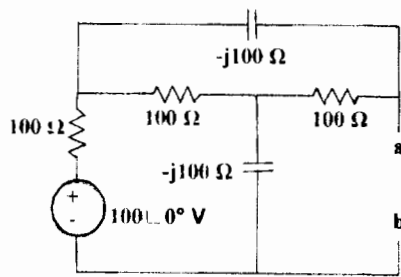


Fig.4

- (e) State and prove Tellegen's theorem.

3 Attempt any two parts : 10×2=20

- (a) Write the necessary condition for driving point function and transfer function.
- (b) Determine voltage transfer function  $V_2(s)/V_1(s)$  for the network shown in Fig. 5

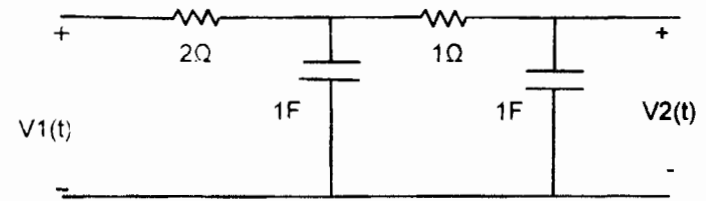


Fig.5

- (c) For the ladder network shown in Fig. 6 find
- (i) Driving point input impedance
  - (ii) Transfer impedance function  $V_2/I_1$

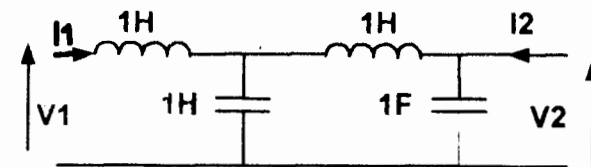


Fig.6

4 Attempt any two parts :

10×2=20

- (a) For the network shown in Fig. 7, Find Z-Parameter and hence find transmission parameter.

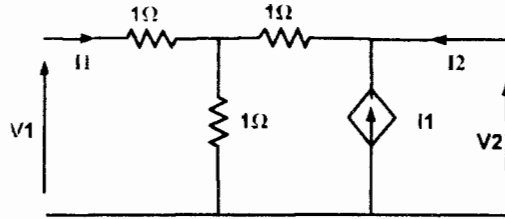


Fig.7

- (b) Explain the reciprocity condition for two port network. Also derive the condition for reciprocity for Z, T and h-parameter.
- (c) Find Y parameter for the network shown in Fig. 8

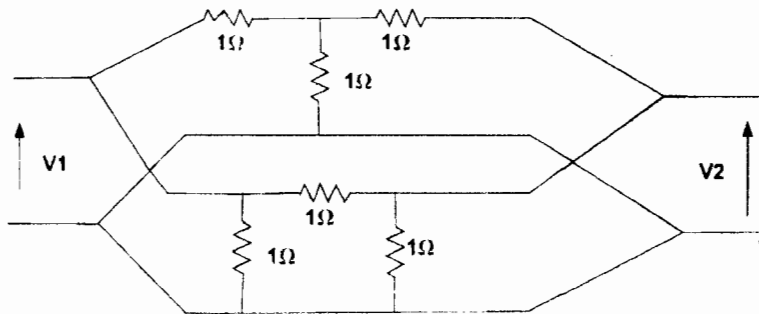


Fig.8

5 Attempt any two parts :

10×2=20

- (a) Design a constant k low pass T section filter to be terminated in  $600 \Omega$ , having cutoff frequency of 3 kHz. Determine :
- The frequency at which the filter is 17.372 dB.
  - Attenuation at 6 kHz.
  - The characteristic impedance and phase constant at 2 kHz.
- (b) An impedance function has the pole and zero diagram shown in Fig. 9. Find impedance function if  $Z(-4)=3/8$  and realize it in Cauer I and Cauer-II form

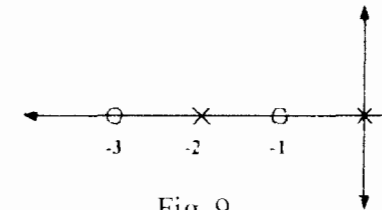


Fig. 9

- (c) State the properties of RL driving point impedance function. Also realize the given network impedance function using Foster form I

$$Z(s) = \frac{(s+1)(s+3)}{(s+2)(s+4)}$$