

5. Attempt any two parts : (10×2=20)
- Explain the operation of series voltage regulator.
  - How SMRS is different from linear feedback regulator ? Give various applications.
  - What is the difference between an 7808 and an 7908 IC regulator ? What is the difference in circuit connections, if they are both used to produce an 8V regulated supply ?



Printed Pages—4

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3086

Roll No.

**B. Tech.**

(SEM. V) ODD SEMESTER THEORY EXAMINATION  
2010-11


### ANALOG INTEGRATED CIRCUITS

Time : 3 Hours

Total Marks : 100

Note : Attempt all the questions.

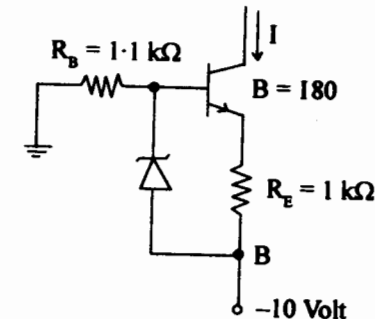
1. Attempt any four parts : (5×4=20)
- Explain brief view of differential amplifier.
  - What is the level translator circuit ? What is its significance in a cascade differential amplifier ?
  - Calculate current  $I$  in the circuit of figure 1.



- Draw the block diagram of an OP-Amp and describe its various blocks.
- Discuss the operation and significance of a multiple output transistor current mirror.
- What is primary advantage of using an active load.

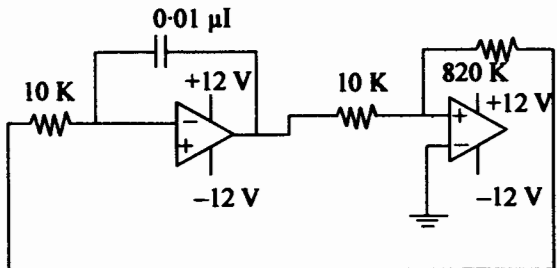2. Answer any four parts : (5×4=20)

- Why timer IC was given the name IC555. What are its essential building blocks ? Explain them.
- Calculate the amplitude of the triangular wave and square wave for fig. (a).




- Explain the difference between capture and lock range of frequencies of the PLL with suitable examples.
- Explain crystal controlled oscillator.
- Determine the frequency and duty cycle for 555 astable multivibrator output for  $C = 0.01 \mu F$ ,  $R_A = 2.2 k\Omega$  and  $R_B = 3.901 k\Omega$ .
- Design a Wein bridge oscillator that will oscillate at 2 kHz.

3. Attempt any two parts : (10×2=20)

- What is meant by filter ? Give the classification of the filters. What are the advantages of an active filter over a passive filter ?
- Write short notes on any two :
  - Second order active filter method
  - High order filters
  - State variable filter.

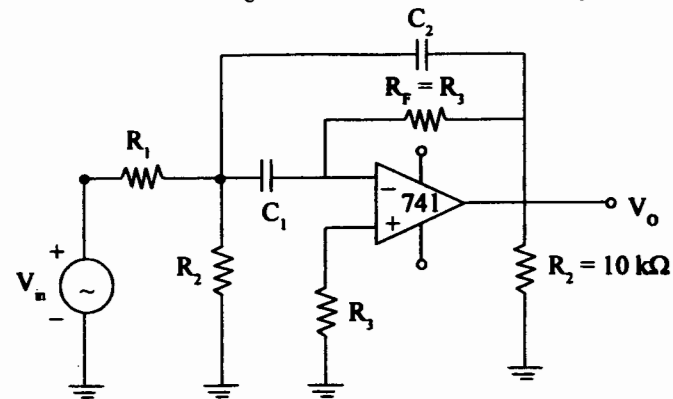(c) Design a Bandpass filter using the op-amp 741 shown below, so that  $F_c = 1 \text{ KHz}$ ,  $Q = 3$  and gain  $A_f = 10$ .



4. Answer any two parts : (10×2=20)

- Explain the hysteresis loop obtained in the Schmitt trigger operation.
- Draw a sample-and-hold circuit. Explain its operation briefly.
- Given a circuit of Fig. which gives square wave output. Find R and C so that square wave with period 10 m secs can be generated.

