

to peak) at 1 kHz and $V_{S2} = 40$ mV (peak to peak) at 1 kHz for the differential amplifier shown in figure 2. Assume the transistor is made of silicon with $h_{ie} = 3.2$ k Ω .

 


Figure 2

- (c) Explain the operation of differential MOS pair :
- When common-mode input voltage
 - When a differential input voltage.
5. Attempt any *two* parts of the following : (10×2=20)
- Sketch the block diagrams of negative feedback arrangements. Derive an expression for gain with negative feedback.
 - Show that the gain bandwidth product of an amplifier with negative feedback is the same as that of an amplifier without feedback.
 - Draw the circuit of phase-shift oscillator and explain its working. State the advantage and disadvantages of this oscillator.

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0321

Roll No.

B. Tech.

(SEM. IV) THEORY EXAMINATION 2011-12

ELECTRONIC CIRCUITS

Time : 3 Hours

Total Marks : 100

Note : Attempt *all* questions. Each question carries equal marks.

- Attempt any *four* parts of the following : (5×4=20)
 - Sketch an op-amp noninverting amplifier circuit. Explain the operation of the noninverting amplifier and derive an equation for its voltage gain.
 - Explain common mode voltage, common mode voltage gain and common mode rejection ratio for operational amplifiers.
 - Write equations for input impedance, output impedance and voltage gain for the noninverting amplifier.
 - Sketch the circuit of a three input inverting summing amplifier. Explain the operation of the circuit and derive an equation for the output voltage.
 - Explain the characteristics of ideal operational amplifier. What is the concept of virtual ground in op-amp ?
 - Sketch an op-amp difference amplifier circuit. Explain the operation of the circuit and derive an equation for the output voltage.

2. Attempt any **four** parts of the following : (5×4=20)

- Explain the constructional detail of a MOSFET.
- Explain the enhancement type n MOSFET with suitable diagram.
- The FET is used as a voltage variable resistance. Give explanation.
- Draw and explain V-I characteristic of n-type depletion MOSFET.
- The amplifier of figure 1 utilizes an n-channel FET for which $V_p = -2.0$ V, $g_{m0} = 1.60$ mA/V and $I_{DSS} = 1.65$ mA. It is desired to bias the circuit at $I_D = 0.8$ mA using $V_{DD} = 24$ V. Assume $r_d \gg R_d$, find (i) V_{GS} , (ii) g_m , (iii) R_S .

 


Figure 1

- Draw the circuit of CS amplifier of MOSFET with the help of small signal equivalent circuit and find out the expression for voltage gain and output impedance.

3. Attempt any **two** parts of the following : (10×2=20)

- Sketch a family of CB output characteristics for a transistor. Indicate the active, cutoff and saturation regions.
 - What is meant by load line of a transistor? Explain with a simple circuit diagram consisting of an NPN transistor.
- Why is potential divider biasing preferred over all other biasing circuit? A CE amplifier employing an NPN transistor has load resistor R_C connected between collector and V_{CC} supply of +16 V. For biasing a resistor R_1 is connected between collector and base. Resistor $R_2 = 30$ k Ω is connected between base and ground and resistor $R_E = 1$ k Ω is connected between emitter and ground. Draw the circuit diagram. Calculate the values of R_1 and R_C if $V_{BE} = 0.2$ V, $I_E = 2$ mA, $\alpha_o = 0.985$ and $V_{CE} = 6$ V.
- Draw the circuit of an RC coupled amplifier. Draw its gain V/s frequency characteristics and indicate cut-off frequency and bandwidth.

4. Attempt any **two** parts of the following : (10×2=20)

- What is the differential amplifier? Explain the working with suitable diagram. Why matched transistors are required in a differential amplifier?
- Calculate the operating point values, differential gain, common mode gain, CMRR, output if $V_{s1} = 60$ mV (peak