

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2498

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. VI) EVEN THEORY EXAMINATION 2012-13

POWER SYSTEM ANALYSIS

Time : 3 Hours

Total Marks : 100

Note :- Attempt all questions. Each question carries equal marks.

1. Answer any two parts of the following : (10×2=20)

(a) What do you understand by "Per Unit System" in power system analysis? What are the importance and limitations of per unit system?

(b) The line currents in a 3 ϕ supply to an unbalanced load are respectively :


$$I_a = 10 + j 20 \text{ Amp}$$

$$I_b = 12 - j 10 \text{ Amp and}$$

$$I_c = -3 - j 5 \text{ Amp.}$$

The phase sequence is abc. Determine the sequence components of currents.

(c) A 50 Hz, 50 mVA, 13.2 kV star-grounded alternator is connected to a line through a Δ/Y transformer as shown in figure-1.

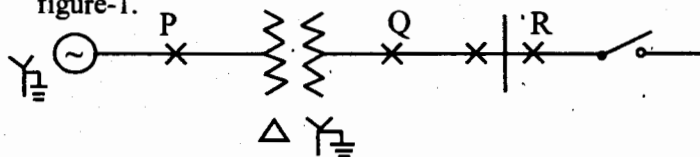**Figure-1**

The positive, negative and zero sequence impedances of the alternator are $j 0.1$, $j 0.1$ and $j 0.05$ p.u. respectively.

The transformer rated at 13.2 kV Δ /120 kVY, 50 MVA with star solidly grounded has the sequence impedances of $X'' = X_2 = X_0 = j 0.1$ p.u. each. The line impedances between Q and R are $X'' = j 0.03$, $X_2 = j 0.03$ and $X_0 = j 0.09$ p.u. respectively. Assuming the fault to take place at P, determine the subtransient fault current for :

- (i) 3- ϕ fault
- (ii) a line-to-ground fault
- (iii) a line-to-line fault
- (iv) a double line to grounded fault.

Also express fault currents as a % of 3- ϕ fault current as calculated in (i).

2. Answer any **two** parts of the following : **(10 \times 2=20)**

- (a) What do you mean by "Unsymmetrical Fault" in P.S.A ?
What are the drawbacks of unsymmetrical fault in power system analysis ?
- (b) Explain the line-to-line fault on an unloaded generator and power system network with and without fault impedances.
- (c) Discuss the computer methods for short-circuit calculations in 3- ϕ unsymmetrical faults. What are the advantages and disadvantages of this method ?

3. Answer any **two** parts of the following : **(10 \times 2=20)**

- (a) Explain the following :
 - (i) Reference Bus or Slack Bus.

(ii) Voltage Controlled Bus or Generator Bus.

(iii) Load Bus.

Also mention their importance.

(b) Consider the power system network as shown in figure-2 :

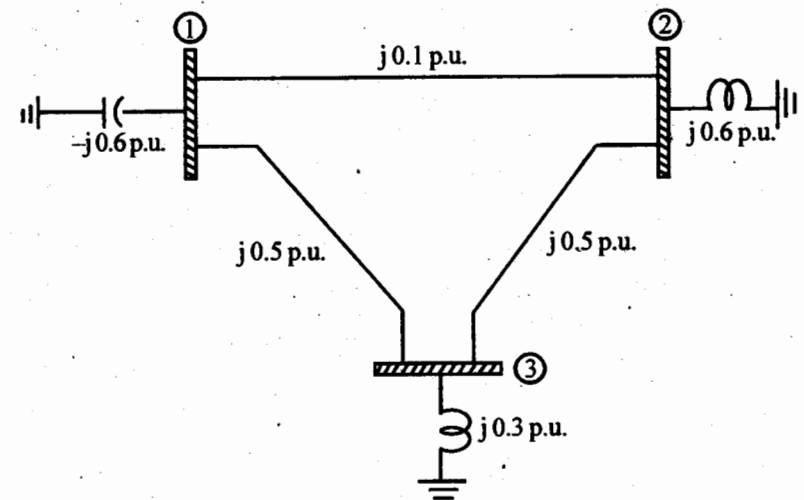


Figure-2

Determine Y_{BUS} matrix for above power system network shown in figure-2.

- (c) Explain the algorithms of Newton-Raphson method. What are the advantages and disadvantages of Newton-Raphson method over Gauss Siedal method ?

4. Answer any **two** parts of the following : **(10 \times 2=20)**

- (a) Explain the following :
 - (i) Voltage Stability

(ii) Rotor Angle Stability.

Also mention their importance in power system networks.

- (b) What do you mean by "Swing Equation" in power system networks ? What is the importance swing equations in power system networks ? Also mention its drawbacks. What are the factors affecting steady state and transient stability and methods of improvement ?
- (c) Discuss the transient stability studies by equal area criterion and step-by-step method.

5. Answer any **two** parts of the following : (10×2=20)

- (a) Explain the Bewlag's Lattice Diagram. What is the importance of Bewlag's Lattice Diagram in power system analysis ? Also mention its limitations.
- (b) Show that a travelling wave moves with a velocity of light on the overhead line and its speed is proportional to $\frac{1}{\sqrt{\epsilon r}}$ on a cable with dielectric material of permittivity ϵr .
- (c) Explain with neat sketches the mechanism of lightning discharge. Differentiate between a hot lightning stroke and a cold lightning stroke.